Concept Question 10-10: Can the *pf*-compensation method be used in single-phase circuits be extended to a three-phase source connected to a balanced three-phase load?

Yes, as illustrated by Fig. 10-14.

