

Concept Question 8-10: To achieve maximum transfer of power from a source circuit to a load, how should the impedance of the load be related to that of the source circuit?

$$Z_L = Z_S^* \quad (\text{maximum power transfer}),$$