Concept Question 1-2: What is the difference between analysis and synthesis?

In analysis, we try to figure out how a circuit works, whereas in synthesis, we are given a set of desired operational characteristics and we are asked to design a circuit that meets those characteristics. Synthesis is another name for design.