Concept Question 3-6: What is a supermesh, and how is it used in mesh analysis?

▶ Two adjoining meshes that share a current source constitute a supermesh. The current source may be of the independent or dependent type, and it may include a resistor in series with it, but not in parallel. ◀