Concept Question 8-12: How is power measured in Multisim? Why must all four terminals of the wattmeter be used to obtain a power measurement?

Power can be measured using a wattmeter instrument. A wattmeter measures the voltage across two terminals as well as the current through terminals and calculates $p(t) = i(t) * v(t)$, hence requiring four terminals.